

Single Cycle

Jonathan Windle

University of East Anglia

J.Windle@uea.ac.uk

June 10, 2017

Overview I


- 1 State Machines
- 2 Instruction and Data Memories
- 3 Instruction Fetch
- 4 R-type recap
- 5 Register File and ALU
- 6 Executing R-type Instructions
- 7 I-Type Instruction Recap
- 8 Executing Load/Store Instructions
- 9 ALUSrc Control Signal
- 10 MemToReg Control Signal
- 11 RegDest Control Signal
- 12 Branch Instruction Recap

State Machines

- Computers are state machines
- Built from combinational and state elements
- Combinational element outputs depend only on their inputs
 - e.g. gates, ALU
- State elements hold state i.e. have some internal storage
 - E.g. registers, instruction and data memories
 - **Clocking methodology** defines when data can be read and written
 - We will assume **positive edge-triggered** clocking.
- Edge-triggered clocking methodology allows for reading a state element and writing in the same clock cycle
- The clock needs to be long enough so that the input to the state element is stable before the positive clock edge starts.


Instruction and Data Memories

 - All buses are 32 bits
- Blue connectors represent control signals. **MemWrite** or **MemRead** should be **asserted** (logical high) depending whether we want to write or read from memory
- For simplicity, assume cannot write to instruction memory - program already there.



Instruction Fetch

 - The CPU fetches instructions from the instruction memory and executes them
- The program counter PC stores the address of the current instruction
- We also need an adder to increase PC
 - MIPS instructions are one word long, so the PC should be incremented by four to read the subsequent instruction




R-type recap

- Arithmetic instructions use R-format
- Three-register-addresss instructions for data manipulations:
 - $R:rd \leftarrow \text{funct } rt$


Type	31	format(bits)					0
R	opcode (6)	rs (5)	rt (5)	rd (5)	shamt (5)	funct (6)	

Register File and ALU

 - R-type instructions require registers and ALU
- There are 32 registers in the MIPS register file.
- We need 5 bits to address registers
- We have 5 operations to encode so ALUop needs to have 3 bits




ALUop	Function
000	and
001	or
010	add
110	sub
111	slt

 

Executing R-type Instructions

 - Instruction is fetched from memory
- **rs** and **rt** registers are read from the register file
- The ALU operates on the data read. ALU function determined by the **funct** field - bits [0:5] of the instruction
- The result is written into the **rd**




I-Type Instruction Recap

- I-type instructions include `lw,sw` and `beq`
- `rt` is the destination for `lw` but a source for both `sw` & `beq`
 - `lw $rt, imm($rs)`
 - `sw $rt, imm($rs)`
 - `beq $rs, $rt, imm`
- `immediate` is a 16-bit signed constant (two's complement)

Type	format(bits)				0
I	opcode (6)	rs (5)	rt (5)	immediate (16)	


Executing Load/Store Instructions

 - For load/store instructions, the base register **rs** is added to the **sign-extended** immediate operand producing a data memory address
- The ALU must accept either a register operand for arithmetic instructions or a sign-extended immediate operand for load/store instructions
- We had to add additional three **multiplexors** with their control signals.




ALUSrc Control Signal

 - When asserted selects an **immediate** operand, otherwise a **register** operand.



MemToReg Control Signal

 
- When asserted selects storing the data **data memory contents** in a register, otherwise it stores the **result of the ALU operation**



RegDest Control Signal

- We need one more mux for selecting the destination register, which is different in R and I-type instructions
- When asserted selects storing the result in a register **rd(R-type)** otherwise it stores the result in the **rt register (lw,l-type)**.

R	opcode (6)	rs (5)	rt (5)	rd (5)	shamt (5)	funct (6)
I	opcode (6)	rs (5)	rt (5)	immediate (16)		

 

Branch Instruction Recap

- In branch instructions the immediate operand is not an address offset, but the instruction offset:

```
beq $a0, $0, Label
    add ...
    add ...
    j Label2
Label: add ...
```

Type	31	format(bits)			0
I	opcode (6)	rs (5)	rt (5)	immediate (16)	

- Label** is three instructions after the instruction immediately following beq, hence the offset will be three words (twelve bytes) i.e. the branch address equals $PC + 4 + \text{imm} \times 4$
- Of course, the offset is a signed integer (two's complement)

The End